

Notes:

I have NOT built this circuit so I can not vouch for its performance.

Reduction of Ip to 20mA change R3 to 80 ohms and R4 to 3.6K, /*7.2K values of Ip below this value are not recommended due to potential noise and linearity problems.

Output can also be transformer coupled if desired, primary about 5K,

2:1 or 1:1

*Operation under these conditions cannot be guaranteed, and plate voltage must be delayed until V1 has warmed up to avoid exceeding Vp. Potential linearity benefit. Pd at limit however...

Tube Spec:

Rp:1.8K

9m: 24K siemens

mu:43

Plate diss:4.0W

Vp-max: 180V